

Interfacing and Memory

Martin Schoeberl

Technical University of Denmark
Embedded Systems Engineering

February 20, 2021

Overview

- ▶ Repeat FSMD (for the vending machine)
- ▶ Interfaces
- ▶ Memory (intern and extern)
- ▶ Serial interface (RS 232)
- ▶ 2 hours lab SRAM exercise
 - ▶ Exercise description is in DTU Inside
 - ▶ [sram_exercise.pdf](#)
 - ▶ [SRAM data sheet: CYCC1041...](#)
- ▶ The course evaluation is open for feedback

The Online Exam

- ▶ We will use the “old” online system
- ▶ Show it at <http://onlineeksamen.dtu.dk/>
- ▶ It will be two parts:
 - ▶ Multiple choice
 - ▶ Download and hand in a document (e.g., PDF generated from Word)
- ▶ You can play with the very short one today
- ▶ We will do a test exam next week, before the lab

Using an FSM and a Datapath


- ▶ About the design of the vending machine (VM)
- ▶ Some of you start coding the VM directly
 - ▶ This may work for small designs
 - ▶ But does not scale
- ▶ Better use a systematic approach
- ▶ Use a FSM that communicates with a datapath (FSMD)
- ▶ We will quickly repeat FSMD

Finite-State Machine (FSM)


- ▶ Has a register that contains the state
- ▶ Has a function to computer the next state
 - ▶ Depending on current state and input
- ▶ Has an output depending on the state
- ▶ Use a Moore FSM for the VM

Basic Finite-State Machine

 - ▶ A state register
- ▶ Two combinational blocks



State Diagram

 

- ▶ States and transitions depending on input values
- ▶ Example is a simple alarm FSM
- ▶ Nice visualization
- ▶ Draw the state diagram for your VM during the design
- ▶ Include a state diagram in the report

The Input and Output of the Alarm FSM

- ▶ Two inputs and one output

```
val io = IO(new Bundle{  
    val badEvent = Input(Bool())  
    val clear = Input(Bool())  
    val ringBell = Output(Bool())  
})
```


Encoding the State

- ▶ We can optimize state encoding
- ▶ Two common encodings are: binary and one-hot
- ▶ We leave it to the synthesize tool
- ▶ Use symbolic names with an Enum
- ▶ Note the number of states in the Enum construct
- ▶ We use a Scala list with the :: operator

```
val green :: orange :: red :: Nil = Enum(3)
```

Start the FSM

- ▶ We have a starting state on reset

```
val stateReg = RegInit(green)
```

The Next State Logic

```
switch (stateReg) {  
  is (green) {  
    when(io.badEvent) {  
      stateReg := orange  
    }  
  }  
  is (orange) {  
    when(io.badEvent) {  
      stateReg := red  
    } .elsewhen(io.clear) {  
      stateReg := green  
    }  
  }  
  is (red) {  
    when (io.clear) {  
      stateReg := green  
    }  
  }  
}
```

The Output Logic

```
io.ringBell := stateReg === red
```

Summary on the Alarm Example

- ▶ Three elements:
 1. State register
 2. Next state logic
 3. Output logic
- ▶ This was a so-called Moore FSM
- ▶ There is also an FSM type called Mealy machine

FSM with Datapath

- ▶ A type of computing machine
- ▶ Consists of a finite-state machine (FSM) and a datapath
- ▶ The FSM is the master (the controller) of the datapath
- ▶ The datapath has computing elements
 - ▶ E.g., adder, incrementer, constants, multiplexers, ...
- ▶ The datapath has storage elements (registers)
 - ▶ E.g., sum of money payed, count of something, ...
- ▶ You VM design shall be a FSMD


FSM-Datapath Interaction

- ▶ The FSM controls the datapath
 - ▶ For example, add 2 to the sum
- ▶ By controlling multiplexers
 - ▶ For example, select how much to add
 - ▶ Not adding means selecting 0 to add
- ▶ Which value goes where
- ▶ The FSM logic also depends on datapath output
 - ▶ Is there enough money payed to release a can of soda?
- ▶ FSM and datapath interact


Popcount Example

- ▶ An FSMD that computes the popcount
- ▶ Also called the Hamming weight
- ▶ Compute the number of '1's in a word
- ▶ Input is the data word
- ▶ Output is the count

Popcount Block Diagram

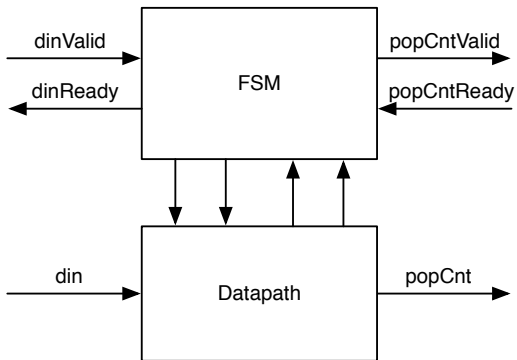


The FSM

 

- ▶ A Very Simple FSM
- ▶ Two transitions depend on input/output handshake
- ▶ One transition on the datapath output

The Datapath

 

Let's Explore the Code

- ▶ In `PopCount.scala`

Usage of an FSMD

- ▶ Of course for your VM
 - ▶ The VM is a simple processor
 - ▶ But not Turing complete
 - ▶ Can *only* process coins of 2 and 5
- ▶ An FSMD can be used to build a processor
- ▶ Fine for simple processors
- ▶ E.g., [Lipsi](#)
- ▶ Pipelined processor topic of
 - ▶ Computer Architecture Engineering (02155)

Use a FSMD for the VM

- ▶ This is the main part your vending machine
- ▶ Can be design and tested just with Chisel testers (no FPGA board needed)
- ▶ See the given tester
 - ▶ Sets the price to 7
 - ▶ Adds two coins (2 and 5)
 - ▶ Presses the buy button
- ▶ Extend the test along the development
 - ▶ Remember test driven development?
 - ▶ Maybe write the test before the implementation
 - ▶ Maybe test developer and FSMD developer are not always the same person

Code Snippets for the VM

```
val idle :: add2 ... :: Nil = Enum(?)
val stateReg = RegInit(idle)
...
switch (stateReg) {
  is (idle){
    when(coin2) {
      stateReg := ...
    }
    when(...) {
      ...
    }
  }
  switch(stateReg) {
    is (add2) { ... } // drive the datapath for
                      adding a coin of kr. 2
  }
}
```

Memory

- ▶ Registers are storage elements == memory
- ▶ Just use a Reg of a Vec
- ▶ This is 1 KiB of memory

```
val memoryReg = Reg(Vec(1024, UInt(8.W)))  
// writing into memory  
memoryReg(wrAddr) := wrData  
// reading from the memory  
val rdData = memoryReg(rdAddr)
```

- ▶ Simple, right?
- ▶ But is this a good solution?

A Flip-Flop

- ▶ Remember the circuit of a register (flip-flop)?
- ▶ Two latches: **master and slave**
- ▶ One (enable) latch can be built with 4 NAND gates
- ▶ a NAND gate needs 6 transistors, an inverter 2 transistors
- ▶ A flip-flop needs 20 transistors (for a single bit)
- ▶ Can we do better?

A Memory Cell

- ▶ A single bit can be stored in 6 transistors
- ▶ That is how larger memories are built
- ▶ FPGAs have this type of on-chip memories
- ▶ Usually many of them in units of 2 KiB or 4 KiB
- ▶ We need some Chisel code to represent it
- ▶ More memory needs an extra chip
- ▶ Then we need to interface this memory from the FPGA

SRAM Memory

- ▶ RAM stands for random access memory
- ▶ SRAM stands for static RAM
- ▶ There is also something called DRAM for dynamic RAM
 - ▶ Uses a capacitor and a transistor
 - ▶ DRAM is smaller than SRAM
 - ▶ But needs refreshes
 - ▶ Different technology than technology for logic
- ▶ All on-chip memory is SRAM (today)


Memory Interface

- ▶ Interface
 - ▶ Address input (e.g., 10 bits for 1 KiB)
 - ▶ Write signal (e.g., we)
 - ▶ Data input
 - ▶ Data output
- ▶ May share pins for the data input and output (tri-state)
- ▶ May have read and write addresses
 - ▶ A so-called dual ported memory
 - ▶ Can do a read and a write in the same clock cycle

On-Chip Memory

- ▶ SRAM by itself is asynchronous
- ▶ No clock, just the correct timing
- ▶ Apply the address and after some time the data is valid
- ▶ But one can add input registers, which makes it a synchronous SRAM
- ▶ Current FPGAs have only synchronous memories
- ▶ FPGAs usually have dual-ported memories
- ▶ This means the result of a read is available on clock cycle after the address is given
 - ▶ This is different from the use of flip-flops (`Reg(Vec(. .))`)

Synchronous Memory

 

Use of a Chisel SyncReadMem

```
class Memory() extends Module {  
  val io = IO(new Bundle {  
    val rdAddr = Input(UInt(10.W))  
    val rdData = Output(UInt(8.W))  
    val wrEna = Input(Bool())  
    val wrData = Input(UInt(8.W))  
    val wrAddr = Input(UInt(10.W))  
  })  
  
  val mem = SyncReadMem(1024, UInt(8.W))  
  
  io.rdData := mem.read(io.rdAddr)  
  
  when(io.wrEna) {  
    mem.write(io.wrAddr, io.wrData)  
  }  
}
```


Read-During-Write

- ▶ What happens when one writes to and reads from the same address?
- ▶ Which value is returned?
- ▶ Three possibilities:
 1. The newly written value
 2. The old value
 3. Undefined (mix of old and new)
- ▶ Depends on technology, FPGA family, ...
- ▶ We want to have a defined read-during-write
- ▶ We add hardware to *forward* the written value

Condition for Forwarding

- ▶ If read and write addresses are equal
- ▶ If write enable is true
- ▶ Multiplex the output to take the new write value instead of the (old) read value
- ▶ Delay that forwarded write value to have the same timing

Memory with Forwarding

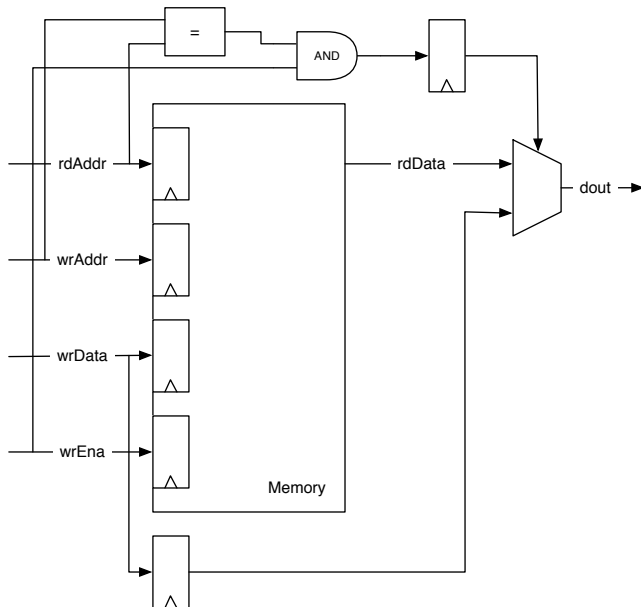

Forwarding in Chisel

```
val mem = SyncReadMem(1024, UInt(8.W))

val wrDataReg = RegNext(io.wrData)
val doForwardReg = RegNext(io.wrAddr ===
    io.rdAddr && io.wrEna)

val memData = mem.read(io.rdAddr)

when(io.wrEna) {
    mem.write(io.wrAddr, io.wrData)
}

io.rdData := Mux(doForwardReg, wrDataReg,
    memData)
```

External Memory

- ▶ On-chip memory is limited
- ▶ We can add an external memory chip
 - ▶ Is cheaper than FPGA on-chip memory
- ▶ Sadly the Basys3 board has no external memory
- ▶ Simple memory is an asynchronous SRAM

External SRAM

- ▶ We *buy* a CY7C1041CV33
- ▶ Let us look into the [data sheet](#)

Interfacing the SRAM

- ▶ FPGA output drives address, control, and data (sometimes)
- ▶ FPGA reads data
- ▶ The read signal is asynchronous to the FPGA clock
- ▶ Do we need an input synchronizer?

Synchronous Interface

- ▶ Logic is synchroous
- ▶ Memory is asynchronous
 - ▶ How to interface?
- ▶ Output signals
 - ▶ Generate timing with synchronous circuit
 - ▶ Small FSM
- ▶ Asynchronous input signale
 - ▶ Usually 2 register for input synchronization
 - ▶ Really needed for the SRAM interface?
 - ▶ We would loose 2 clock cycles

SRAM Read

- ▶ Asynchronous timing definition (data sheet)
- ▶ But, we know the timing and we trigger the SRAM address from our synchronous design
- ▶ No need to use synchronization registers
- ▶ *Just* get the timing correct
- ▶ Dra the example
 - ▶ Address - SRAM - data
 - ▶ Relative to the FPGA clock

Read Timing Continued

- ▶ Add all time delays
 - ▶ Within FPGA
 - ▶ Pad to pin
 - ▶ PCB traces
 - ▶ SRAM read timing
 - ▶ PCB traces back
 - ▶ Pin to pad
 - ▶ Into FPGA register
- ▶ Setup and hold time for FPGA register
- ▶ Is your today's lab exercise

Connecting to the World

- ▶ Logic in the FPGA
 - ▶ Described in Chisel
 - ▶ Abstracting away electronic properties
- ▶ Interface to the world
 - ▶ Simple switches and LEDs
 - ▶ Did we think about timing?
- ▶ FPGA is one component of the system
- ▶ Need interconnect to
 - ▶ Write outputs
 - ▶ Read inputs
 - ▶ Connect to other chips

Bus Interface

- ▶ Memory interface can be generalized
- ▶ We use a so-called bus to connect several devices
- ▶ Usually a microprocessor connected to devices (memory, IO)
- ▶ The microprocessor is the master
- ▶ A bus is an interface definition
 - ▶ Logic and timing
 - ▶ Electrical interface
- ▶ Parallel or serial data
- ▶ Asynchronous or synchronous
 - ▶ But interface clock is usually not the logic clock

Bus Properties

- ▶ Address bus and data bus
- ▶ Control lines (read and write)
- ▶ Several devices connected
 - ▶ Multiple outputs
 - ▶ Use tri-state to avoid multiple driver
- ▶ Single or multiple master
 - ▶ Arbitration for multiple master
- ▶ Sketch a small microprocessor system

Serial I/O Interface


- ▶ Use only one wire for data transfer
 - ▶ Bits are serialized
 - ▶ That is where you need your shift register
- ▶ Shared wire or dedicated wires for transmit and receive
- ▶ Self timed
 - ▶ Serial UART (RS 232)
 - ▶ Ethernet
 - ▶ USB
- ▶ With a clock signal
 - ▶ SPI, I2C, ...

RS 232

- ▶ Old, but still common interface standard
 - ▶ Was common in 90' in PCs
 - ▶ Now substituted by USB
 - ▶ Still common in embedded systems
 - ▶ Your Basys3 board has a RS 232 interface
- ▶ Standard defines
 - ▶ Electrical characteristics
 - ▶ '1' is negative voltage (-15 to -3 V)
 - ▶ '0' is positive voltage (+3 to +15 V)
 - ▶ Converted by a RS 232 driver to *normal* logic voltage levels

Serial Transmission

 - ▶ Transmission consists of
 - ▶ Start bit
 - ▶ 8 data bits
 - ▶ Stop bit(s)
- ▶ Common baud rate 115200 bits/s



RS 232 Interface

- ▶ Generate bit clock with with counter
 - ▶ Like clock tick generation for display multiplexer
- ▶ Output (transmit)
 - ▶ Use shift register for parallel to serial conversion
 - ▶ Small FSM to generate start bit, data bits, and stop bits
- ▶ Input (receive)
 - ▶ Detect start with the falling edge of the start bit
 - ▶ *Position* into middle of start bit
 - ▶ Sample individual bits
 - ▶ Serial to parallel conversion with a shift register

Chisel Code for RS 232

- ▶ More explanation can be found in section 11.2
- ▶ The code is in the Chisel book
- ▶ [uart.scala](#)
- ▶ Also see example usage in [chisel-examples](#) repo

RS 232 on the Basys3

- ▶ Basys3 has an FTDI chip for the USB interface
- ▶ USB interface for FPAG programming
- ▶ But also to provide a RS 232 to the FPGA
- ▶ You can talk with the Laptop
- ▶ Your VM could write out some text
- ▶ Use the Chisel code I showed you
- ▶ Open a terminal to watch (show it)

Today's Lab

- ▶ Paper & pencil exercises on SRAM interfacing
- ▶ On paper or in a plain text editor
- ▶ As usual, show and discuss with a TA
- ▶ Exercise description is in DTU Inside file sharing
- ▶ [sram_exercise.pdf](#)
- ▶ [SRAM data sheet: CYCC1041...](#)

Summary

- ▶ Use an FSMD for the vending machine and simple processors
- ▶ We need to connect to the world
- ▶ FPGA (or any chip) is only part of a system
- ▶ Bus interface to external devices (e.g., memory)
- ▶ Serial interface to connect systems
 - ▶ E.g., your Basys3 board to the laptop